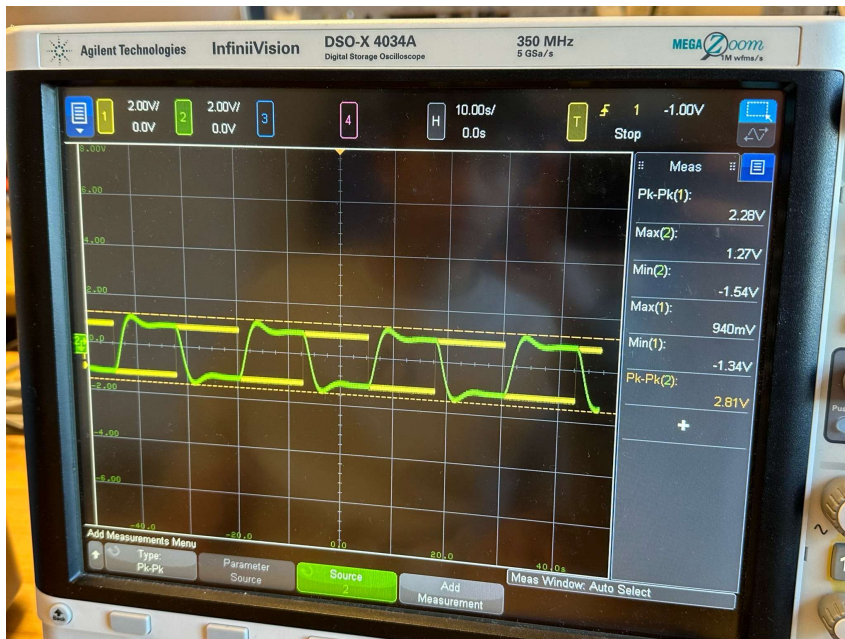



a)


- A 2V pk to pk square wave was used instead of 1V because it gave clearer traces





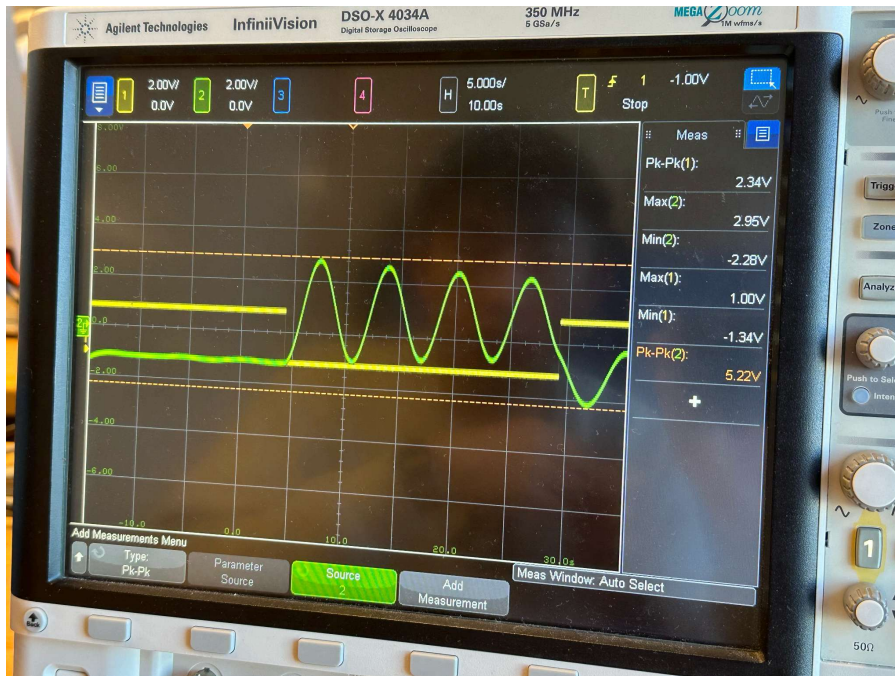- b)
- In shorting R3, damping decreases. The output oscillates, showing underdampness.



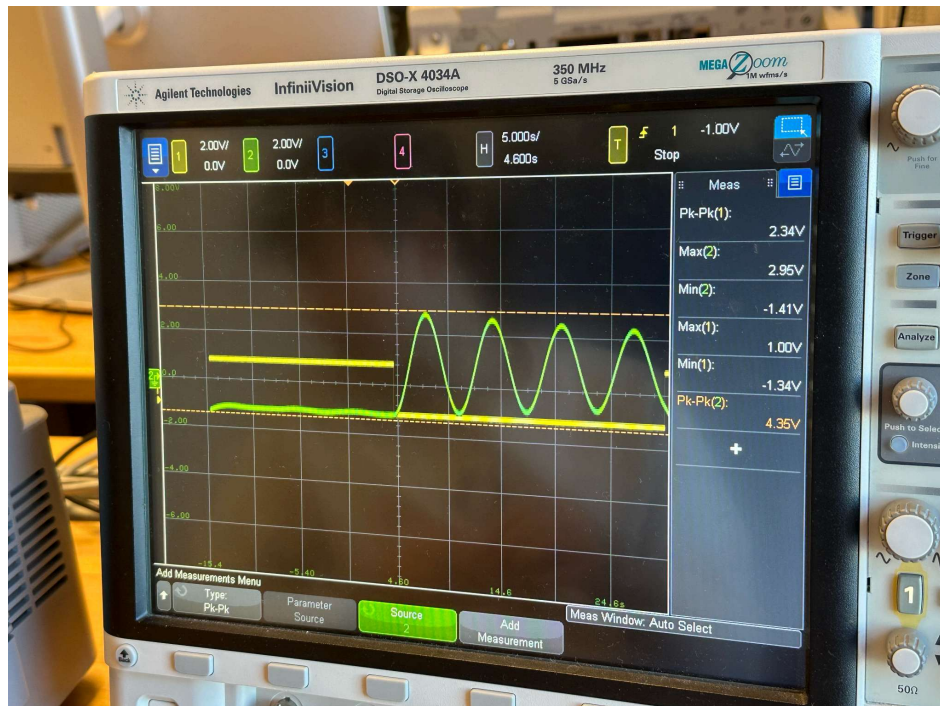

c)

- Critically Damped (as expected, it drops to steady state very quickly):



- Underdamped (0.2 M):



- Overdamped (20M):




d)


- Underdamped ($R_3 = 0.2\text{Meg}$ underdamped case. We also can see the faster frequency of the underdamped oscillations):



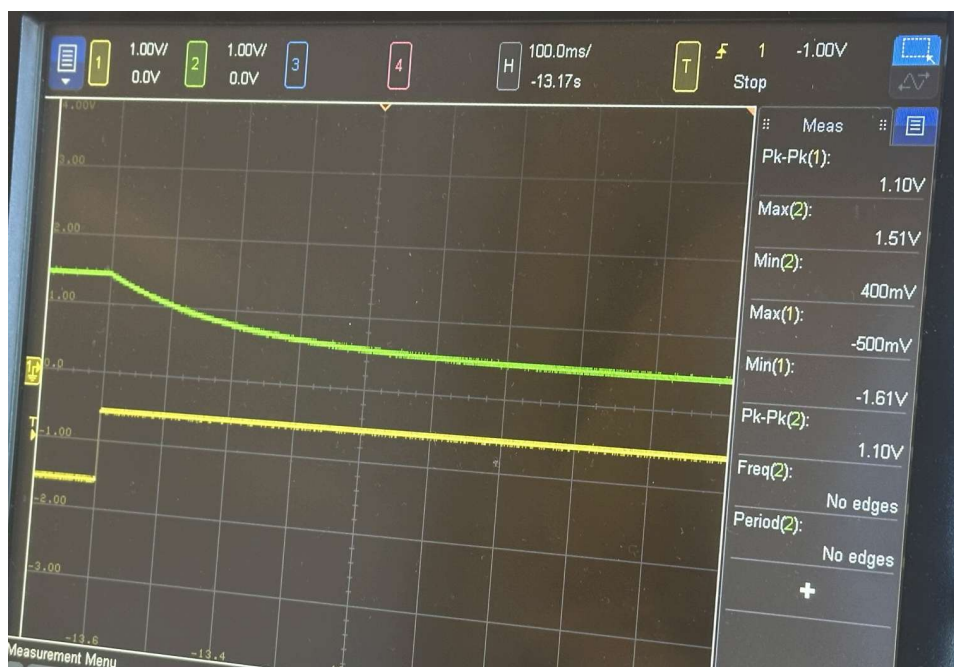- Overdamped Case ($R_3 = 20\text{Meg}$):



- Critically Damped Case:

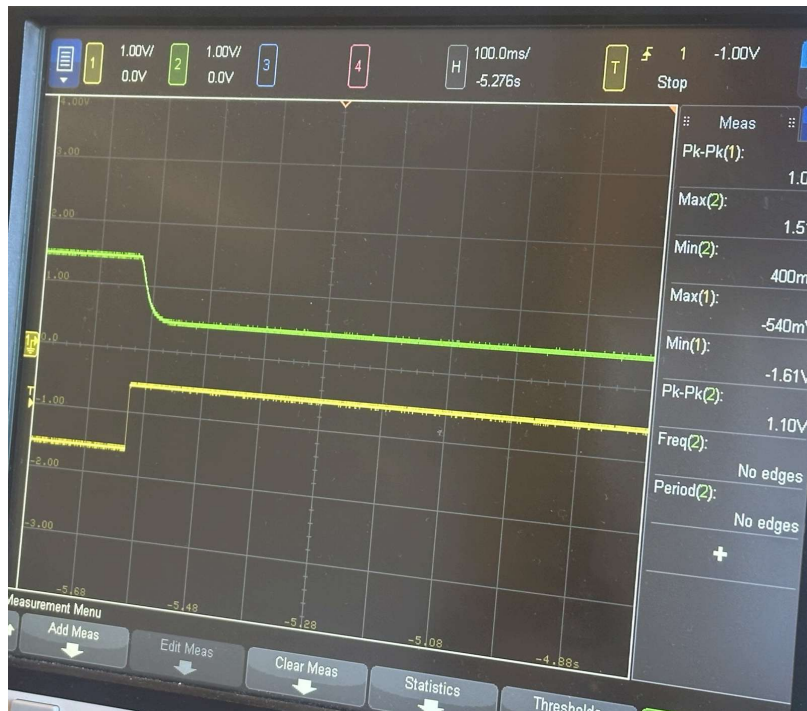

- It can be seen the critically damped case settles to equilibrium much more quickly than the underdamped case.